

CM12002

Computer Systems

Architectures

Sequential Logic

Fabio Nemetz

Sequential Logic

Summary

In this lecture:

- We introduce **sequential** logic circuits, considering the behaviour of a simple **latch** circuit and **flip-flops**

Sequential logic

Logic systems with feedback

- The output of a logic gate in a *combinational* logic system may form the input to a gate 'further down' the system.

In a *sequential* system, the output of a logic gate can also be *fed back* so as to become the input to a gate 'earlier' in the system


- This means that the output may depend not only on the current input, but on *previous inputs* --- **the system has *state*.**

(reference: Stallings book, chapter 12, section 4)

SR Latch (Set-Reset latch)

Input combinations may result in any one of a number of stable or unstable states --- the system may be *nondeterministic*.

 A simple SR (**set-reset**) latch can be implemented with NOR gates:




NOR: truth table

input	output
00	1
01	0
10	0
11	0


SR Latch (Set-Reset Latch)

 - 2 inputs: **S** (Set) and **R** (Reset)
- 2 outputs: Q and Q' (same as $\bar{Q}$) (complements)
- 2 NOR gates connected in a feedback way
- Q is the value we're interested in
- But how does it work?



SR Latch

 - Let's start with **$S = R = 0$** , and **$Q = 0$**
- Lower NOR gate inputs will be $Q=0$ and $S=0 \rightarrow Q'=1$
- Upper NOR gate inputs: $R=0$ and $Q'=1 \rightarrow Q = 0$
- This is consistent and **stable for $S=R=0$**
- The same is valid for **$S = R = 0$** , and **$Q = 1$**




NOR: truth table

input	output
00	1
01	0
10	0
11	0

This circuit can function as a 1-bit memory: **Q** is the value of the bit

SR Latch: Set

 - Let's start again with $S = R = 0$, and $Q = 0$ (we know that $Q' = 1$)
- Now **S (Set) changes to 1**
- Lower NOR gate inputs will be $Q=0$ and $S=1 \rightarrow Q' = 0$
- Upper NOR gate inputs: $R=0$ and $Q' = 0 \rightarrow Q = 1$
- This is consistent and stable for $S=1, R=0$




NOR: truth table

input	output
00	1
01	0
10	0
11	0

SR Latch: Reset

 - Let's assume $S = R = 0$, and $Q = 1$ (we know that $Q' = 0$)
- Now R (Reset) changes to 1
- Upper NOR gate inputs will be $R=1$ and $Q'=0 \rightarrow Q = 0$
- Lower NOR gate inputs: $Q=0$ and $S=0 \rightarrow Q' = 1$
- This is consistent and stable for $S=0, R=1$




NOR: truth table

input	output
00	1
01	0
10	0
11	0

SR Latch

 - What happens if $S=1$ AND $R=1$????
- These inputs are not allowed, because these would produce an inconsistent output (both Q and Q' equal 0).



NOR: truth table

input	output
00	1
01	0
10	0
11	0


SR Latch

Given inputs S and R, and current Q, what's the next state?

Truth tables, in this case, are also called characteristic table


(a) Characteristic Table		
Current Inputs	Current State	Next State
SR	Q_n	Q_{n+1}
00	0	0
00	1	1
01	0	0
01	1	0
10	0	1
10	1	1
11	0	—
11	1	—

(b) Simplified Characteristic Table		
S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	—

 

SR Latch

 
- We can see that time and sequence are involved in this process:
 - S pulses to set Q; after some delay, $Q = 1$
- There is a *delay* before a logic gate responds to an input;
- Two separate gates *cannot* switch *simultaneously*



SR latches are asynchronous or unclocked

Inverted SR Latch

 - It is possible to implement an inverted SR latch using NAND gates
 - you'll see this implementation in some books and even in our lecture notes
- In this case it Sets when $S=0$; Resets when $R=0$
 - can't have $R=S=0$



Redo characteristic tables

Current inputs	Current state	Next state
SR	Q_n	Q_{n+1}
00		
00		
01		
01		
10		
...		

Problems with simple SR Latches

We may observe two problems:

- Asynchronous transitions:
 - in circuits with several sequential components, output states may depend on the order in which changes to inputs occur, or the moment the circuit is tested.

Solution: use a *clock* input to enable/disable transitions, yielding a *gated latch* or *flip-flop*.

- Non-deterministic transitions associated with certain inputs

Solution: avoid states leading to such transitions by *adding gates to control the inputs*.

Flip-flops

Flip-flops introduce a **clock** to latches: this synchronises state transitions across sequential logic circuits

We'll see 3 types of flip-flops: SR, D and J-K

SR flip-flop

AKA Clocked SR flip-flop or Gated SR latch

The simple latch can be extended to be a more useful control circuit by adding a *clock* signal so that the latch responds to inputs **only when the clock signal is present, rather than at any time.**

R and S inputs are passed to the NOR gates only during the clock pulse.

 


Figure 20.24 Clocked S-R Flip Flop

D-type flip-flop (D for data or delay)

- One problem with S–R flip-flop is that the condition $R=1$, $S=1$ must be avoided. One way to do this is to ensure that the two inputs are always different. This is ensured in the D-type flip-flop.
- By using an inverter, the nonclock inputs to the two AND gates are guaranteed to be the opposite of each other.

 


Figure 20.25 D Flip Flop

D	Q_{n+1}
0	0
1	1

- The D flip-flop is referred to as the **data flip-flop** because it is, in effect, storage for one bit of data. The output of the D flip-flop is always equal to the most recent value applied to the input. Hence, it remembers and produces the last input.
- It is also referred to as **the delay flip-flop**, because it delays a 0 or 1 applied to its input for a single clock pulse.

J-K flip-flop

This type of flip-flop makes use of the restricted combination (1,1). It is used to *toggle*, or *change* the output state, of the flip-flop.

 
 


Figure 20.26 J-K Flip Flop

J-K		<table><tr><th>J</th><th>K</th><th>Q_{n+1}</th></tr></table>		J	K	Q_{n+1}									
	J	K	Q_{n+1}												
			<table><tr><td>0</td><td>0</td><td>Q_n</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>$\overline{Q_n}$</td></tr><tr><td>1</td><td>1</td><td>$\overline{Q_n}$</td></tr></table>	0	0	Q_n	0	1	0	1	0	$\overline{Q_n}$	1	1	$\overline{Q_n}$
	0	0	Q_n												
	0	1	0												
1	0	$\overline{Q_n}$													
1	1	$\overline{Q_n}$													

Flip-flops (summary)

S-R

 


Figure 20.24 Clocked S-R Flip Flop

J-K

 


Figure 20.26 J-K Flip Flop

D

 


Figure 20.25 D Flip Flop

 
 
 
Name	Graphical Symbol	Truth Table															
S-R		<table><tr><th>S</th><th>R</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td><td>Q_n</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>—</td></tr></table>	S	R	Q_{n+1}	0	0	Q_n	0	1	0	1	0	1	1	1	—
S	R	Q_{n+1}															
0	0	Q_n															
0	1	0															
1	0	1															
1	1	—															
J-K		<table><tr><th>J</th><th>K</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td><td>Q_n</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>$\overline{Q_n}$</td></tr></table>	J	K	Q_{n+1}	0	0	Q_n	0	1	0	1	0	1	1	1	$\overline{Q_n}$
J	K	Q_{n+1}															
0	0	Q_n															
0	1	0															
1	0	1															
1	1	$\overline{Q_n}$															
D		<table><tr><th>D</th><th>Q_{n+1}</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	D	Q_{n+1}	0	0	1	1									
D	Q_{n+1}																
0	0																
1	1																

Figure 20.27 Basic Flip-Flops


The J-K flip-flop is a *universal* flip-flop:

- it can behave as an SR flip-flop or D flip-flop.

Homework

2.

 - (a) The circuit below uses 3 J-K flip-flops to create an irregular binary counter. Starting with 001 ($Q_2=0$, $Q_1=0$, $Q_0=1$), what are the next 4 3-bit sequences for each clock cycle?



Next time --- using flip-flops